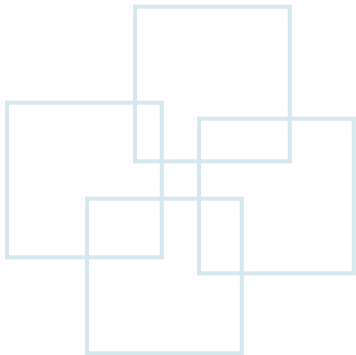






Class 4

Combinational Logic





Three-Input AND and OR

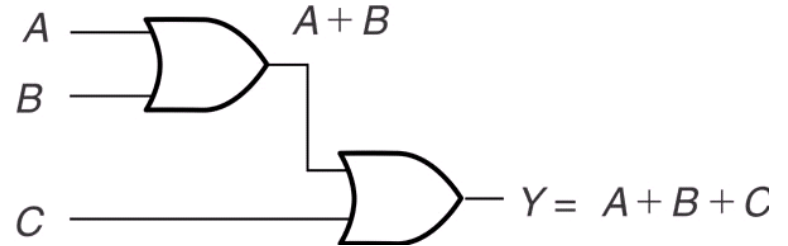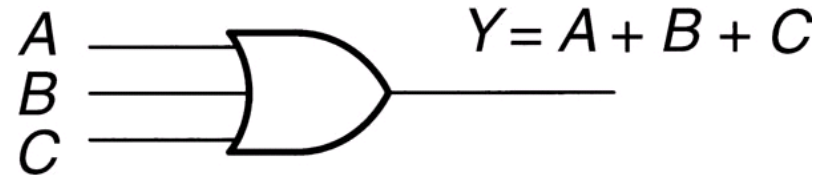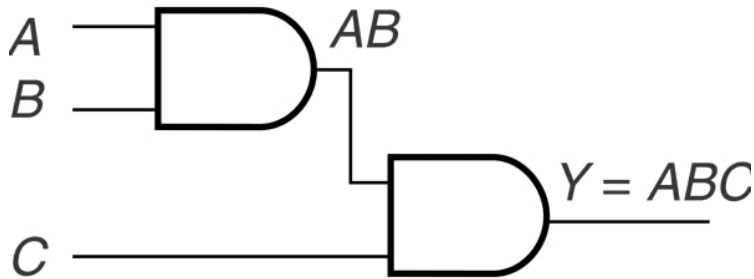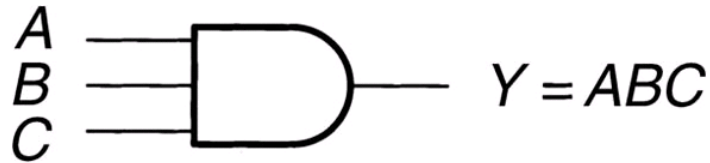





DeMorgan's Theorems

- Break the line and change the sign

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$


$$\overline{A + B} = \overline{A} \cdot \overline{B}$$

A	B	$\overline{A \cdot B}$	$\overline{A + B}$	$\overline{A + B}$	$\overline{A \cdot B}$
0	0	1	1	1	1
0	1	1	1	0	0
1	0	1	1	0	0
1	1	0	0	0	0

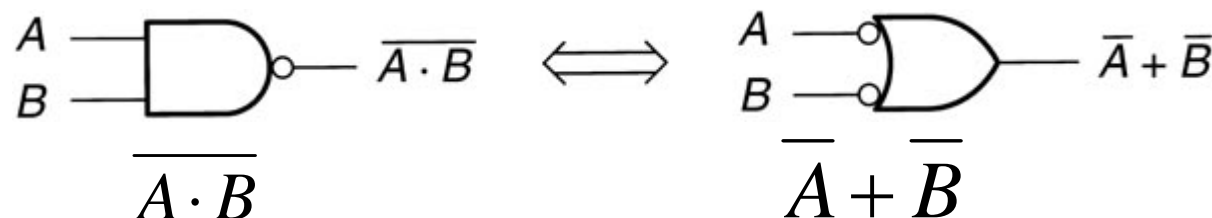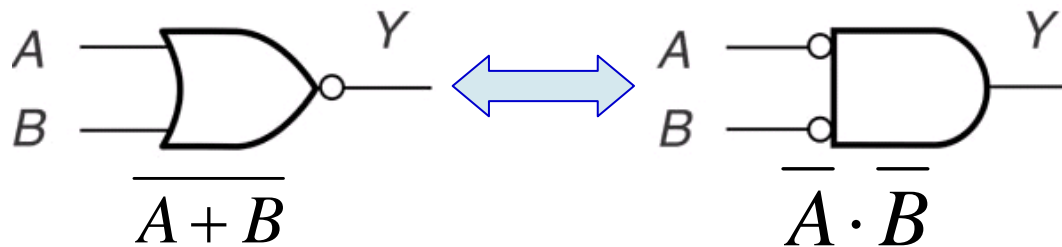



Boolean Expression from Logic Gate

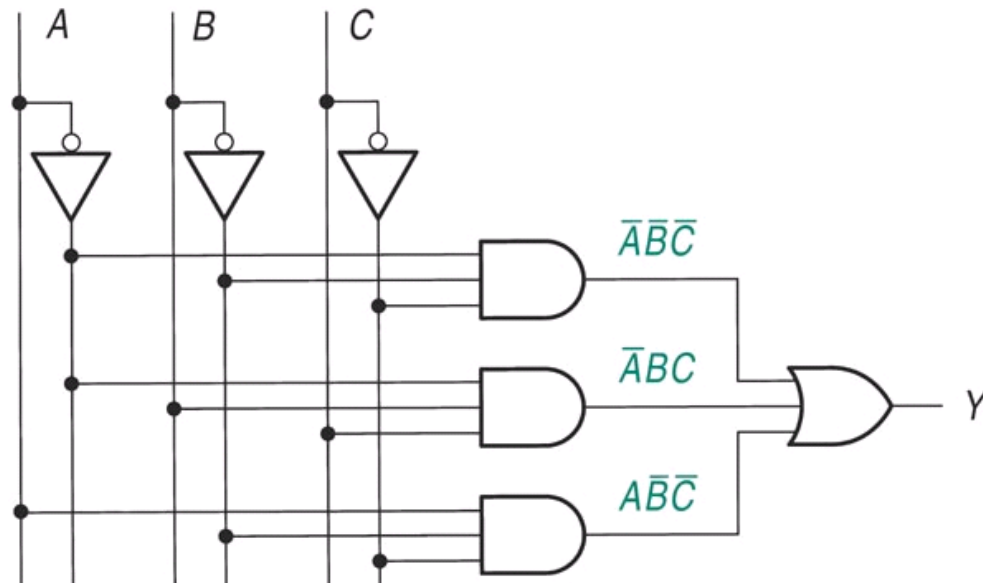

Logic gates

A	B	C	$\overline{A}\overline{B}\overline{C}$	$\overline{A}BC$	$A\overline{B}\overline{C}$	Y
0	0	0	1	0	0	1
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	1	0	1
1	0	0	0	0	1	1
1	0	1	0	0	0	0
1	1	0	0	0	0	0
1	1	1	0	0	0	0

Truth table



Sum of Products (SOP) and Product of Sums (POS)

A	B	C	$\overline{A}\overline{B}\overline{C}$	$\overline{A}B\overline{C}$	$A\overline{B}\overline{C}$	Y	\overline{Y}	Minterms	\overline{Y}	Maxterms
0	0	0	1	0	0	1	0	$\overline{A}\overline{B}\overline{C}$		
0	0	1	0	0	0	0	1		$\overline{A}\overline{B}C$	$A + B + \overline{C}$
0	1	0	0	0	0	0	1		$\overline{A}B\overline{C}$	$A + \overline{B} + C$
0	1	1	0	1	0	1	0	$\overline{A}B\overline{C}$		
1	0	0	0	0	1	1	0	$\overline{A}B\overline{C}$		
1	0	1	0	0	0	0	1		$\overline{A}BC$	$\overline{A} + B + \overline{C}$
1	1	0	0	0	0	0	1		$A\overline{B}\overline{C}$	$\overline{A} + \overline{B} + C$
1	1	1	0	0	0	0	1		ABC	$\overline{A} + \overline{B} + \overline{C}$



Sum of Products (SOP) and Product of Sums (POS) (Cont.)

(SOP) \rightarrow AND then OR

$$Y = \overline{A}BC + A\overline{B}C + ABC$$

$$Y = \overline{B}C + \overline{A}BC \text{ (reduction)}$$


$$\overline{Y} = \overline{\overline{A}BC} + \overline{A\overline{B}C} + \overline{ABC} = \overline{\overline{A}BC} + \overline{A\overline{B}C} + \overline{ABC}$$

$$\overline{\overline{Y}} = \overline{\overline{\overline{A}BC} + \overline{A\overline{B}C} + \overline{ABC}} = \overline{\overline{A}BC} \cdot \overline{A\overline{B}C} \cdot \overline{ABC}$$

$$Y = \overline{\overline{A}BC} \cdot \overline{A\overline{B}C} \cdot \overline{ABC} = (A + B + \overline{C}) \cdot (A + \overline{B} + C) \cdot (\overline{A} + B + \overline{C})$$

$$Y = (A + B + \overline{C}) \cdot (A + \overline{B} + C) \cdot (\overline{A} + B + \overline{C}) \cdot (\overline{A} + \overline{B} + C) \cdot (\overline{A} + \overline{B} + \overline{C})$$


(POS) \rightarrow OR then AND

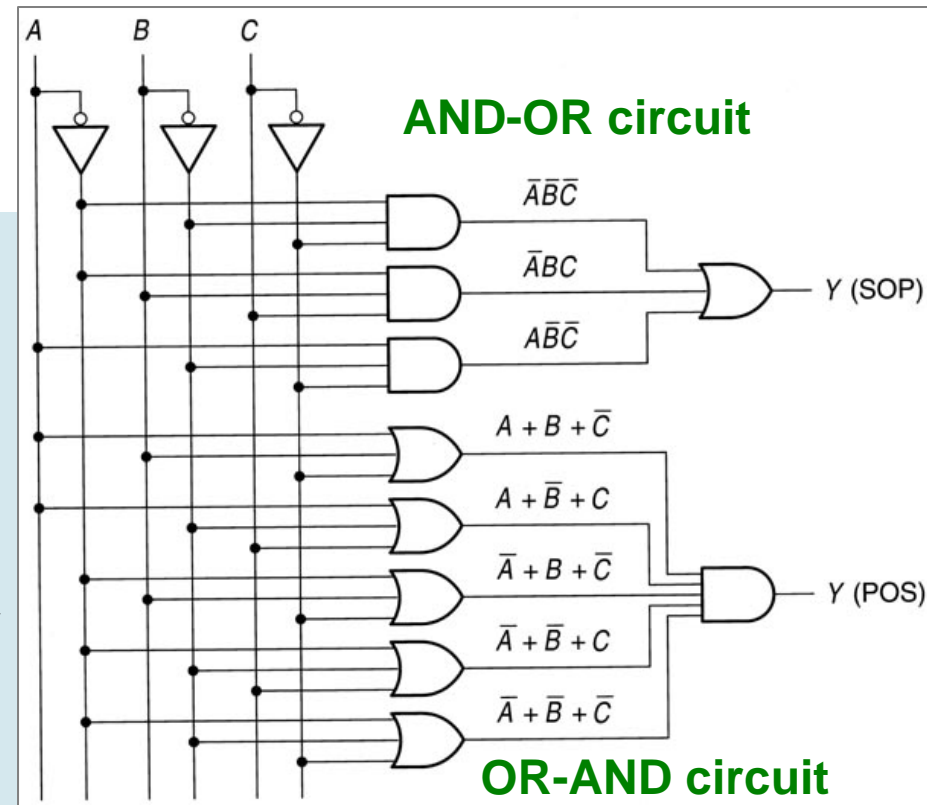



Karnaugh Map (K-Map)

A	B	C	$\overline{A}\overline{B}\overline{C}$	$\overline{A}B\overline{C}$	$A\overline{B}\overline{C}$	Y
0	0	0	1	0	0	1
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	1	0	1
1	0	0	0	0	1	1
1	0	1	0	0	0	0
1	1	0	0	0	0	0
1	1	1	0	0	0	0

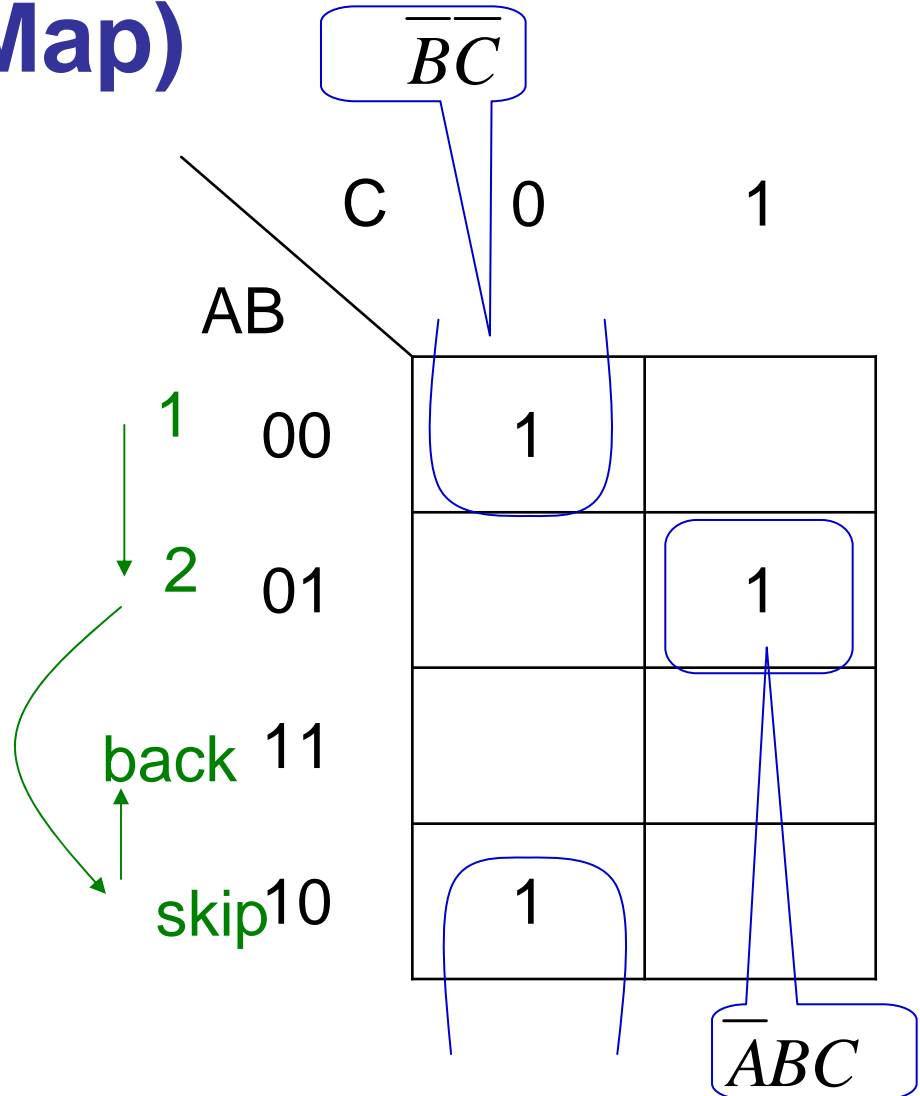




AND-OR Circuit

- Transform the Boolean expression into a simplified SOP(積之和) form.

$$F = \bar{Z} + \bar{X}\bar{Y}$$

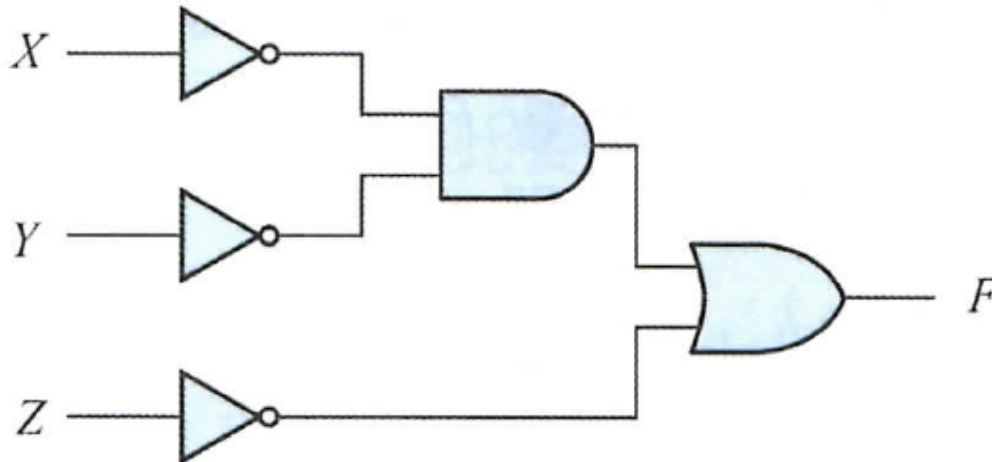

	Z	0	1
XY			
00	1	1	
01	1	0	
11	1	0	
10	1	0	

Annotations: $\bar{Y}\bar{Z}$ points to the cell (00, 1); \bar{Z} points to the column Z=0.




OR-AND Circuit

- Transform the Boolean function into a simplified POS (和之積) form.

$$\overline{F} = XZ + YZ$$
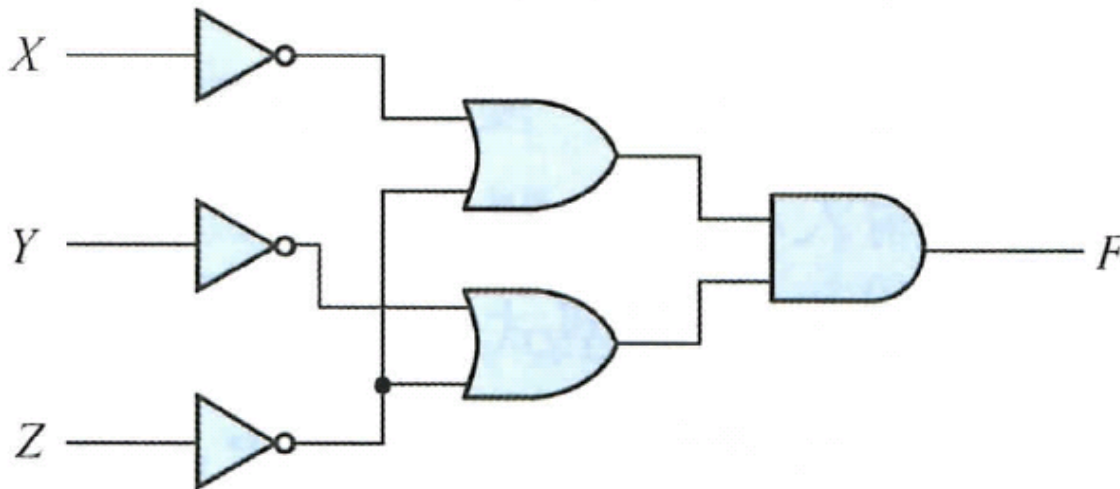
$$F = \overline{XZ + YZ} = \overline{XZ} \cdot \overline{YZ} = (\overline{X} + \overline{Z})(\overline{Y} + \overline{Z})$$



XY	YZ	
	0	1
00	1	1
01	1	0
11	1	0
10	1	0

XZ




AOI (AND-OR-NOT) Circuit


- How to design an AOI circuit:
 - Derive an SOP form for **complement F**
 - Negate the complement F to derive F

$$\overline{F} = XZ + YZ$$

$$F = \overline{XZ + YZ}$$

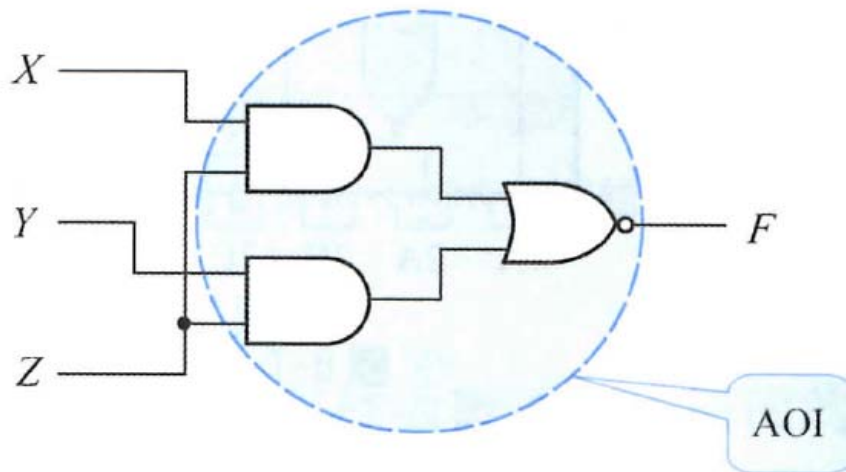



74LS51

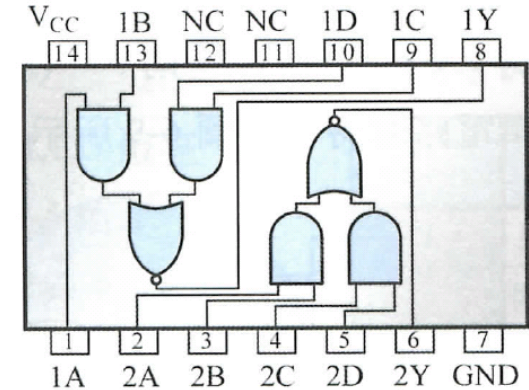

XY		Z	0	1
		YZ		
XY	00	1		1
	01	1		0
	11	1		0
	10	1		0
		XZ		







Four-Input NAND and NOR

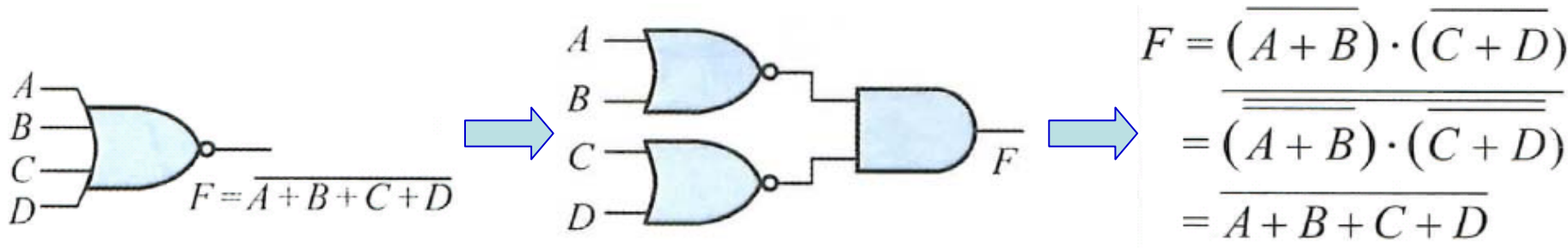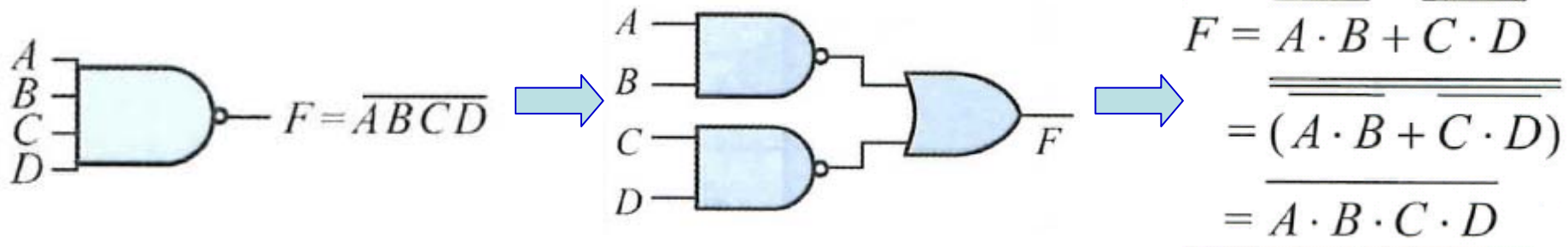






ALL NAND

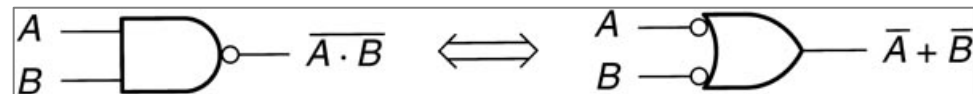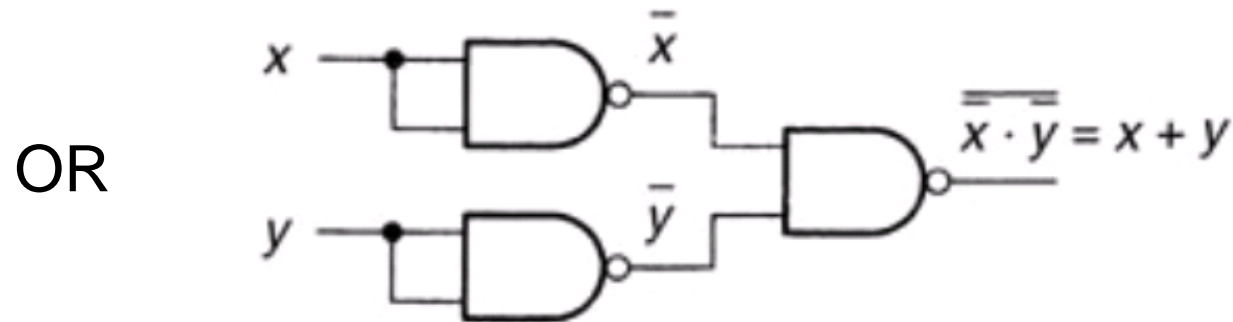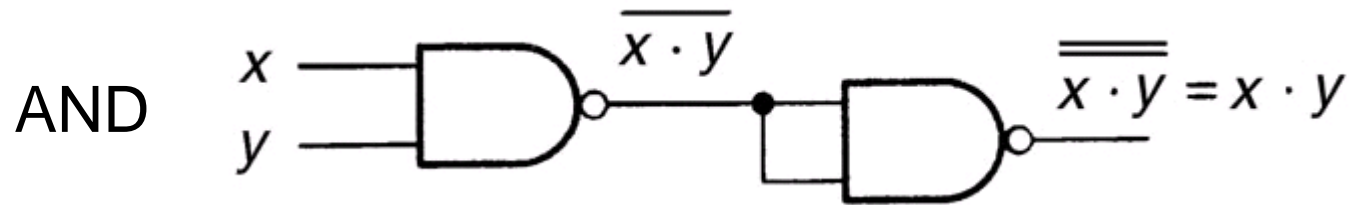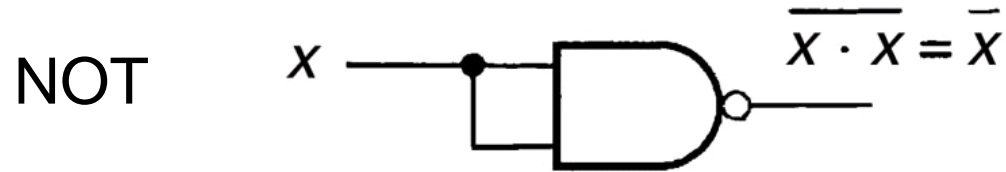



An Example of All NAND


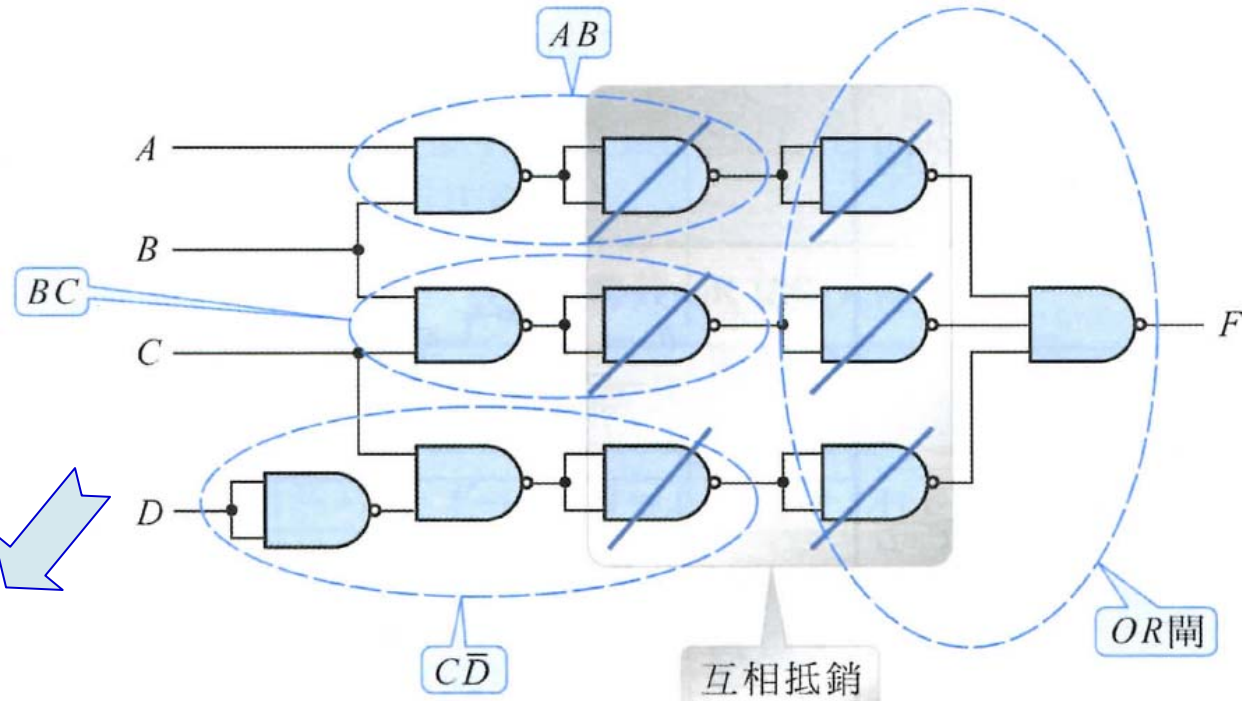
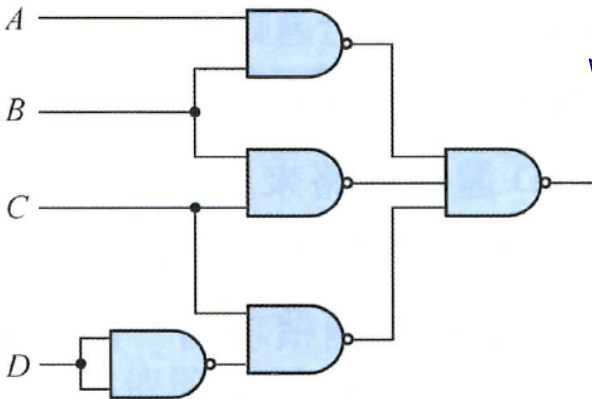
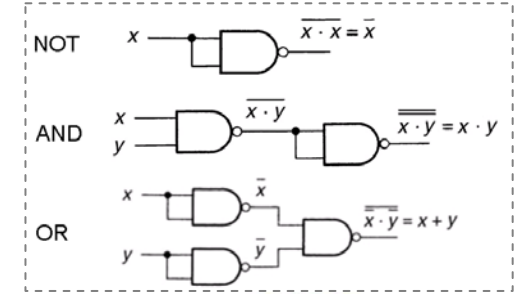
Design an AND-OR circuit in the SOP form so as to derive a simplified circuit.



$$F = AB + BC + C\bar{D}$$






All NOR

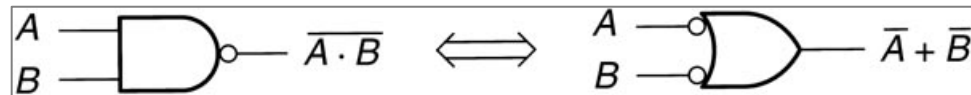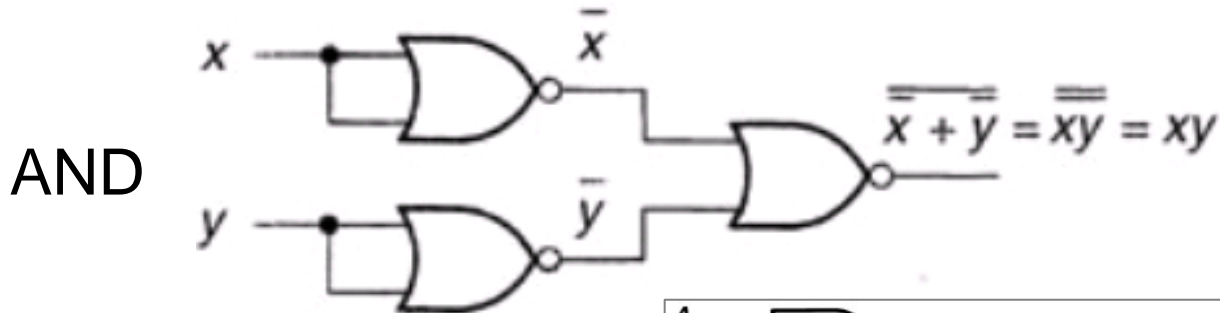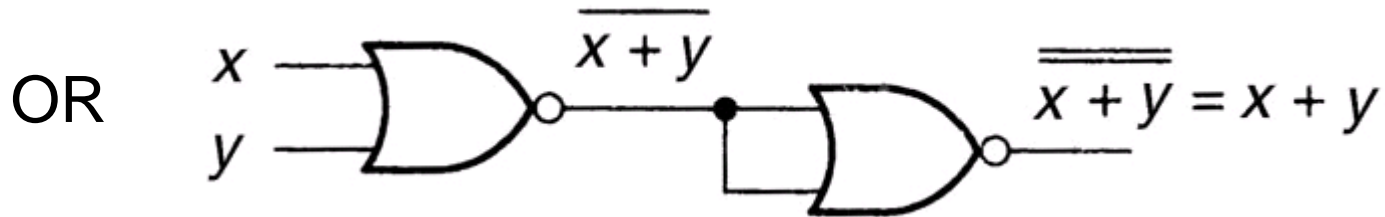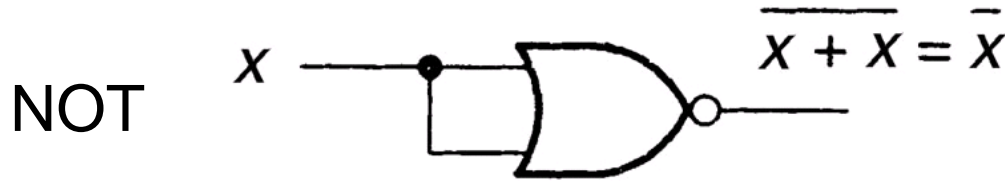



An Example of All NOR

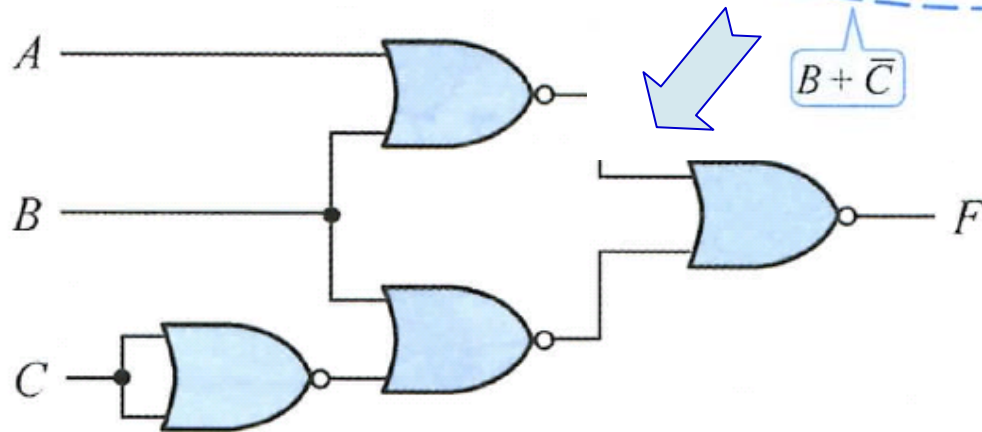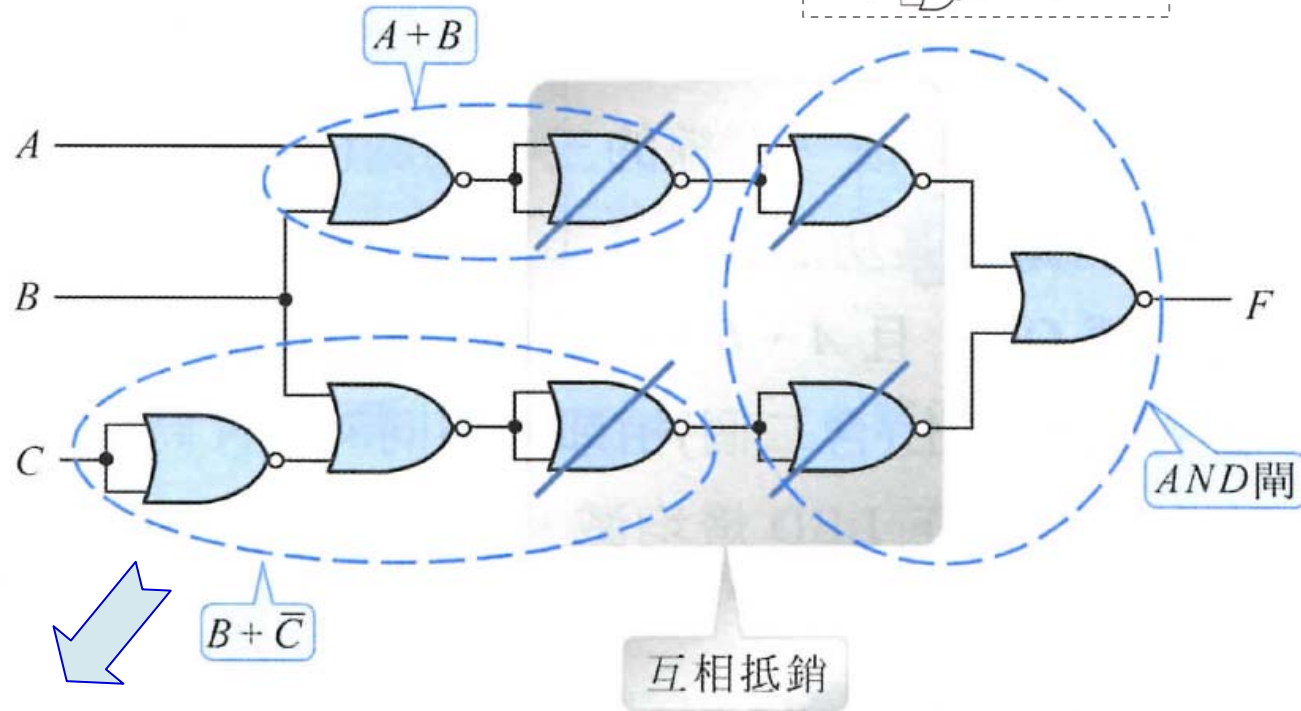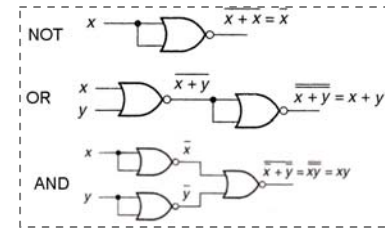Design an OR-AND circuit in the POS form so as to derive a simplified circuit.



$$F = (A + B)(B + \bar{C})$$



Lab 4 – Part 1

- Design a combinational circuit to solve the following question:
 - There are three switches (A, B, and C), one green LED, and one red LED.
 - When the power is on,
 - The red LED is off and the green LED is on when none or one of the switches is on.
 - The red LED is on and the green LED is off when two or three switches are on.




Lab 4 – Part 2


- Design a combinational circuit to solve the following question:
 - There are three switches (A, B, and C) and one LED.
 - When the power is on,
 - The LED is on when any two or more adjacent switches are on at the same time (i.e., A B on, B C on, A B C on).
 - Otherwise, the LED is off.




Chip Logic Circuit

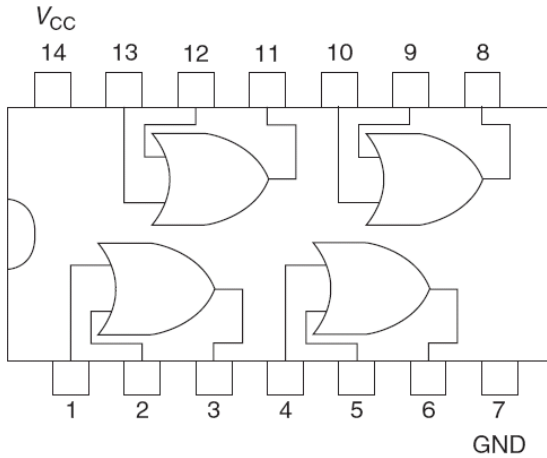

74LS32

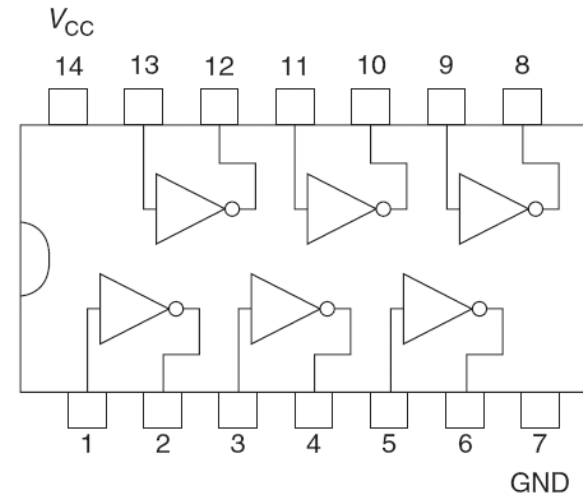


74LS04

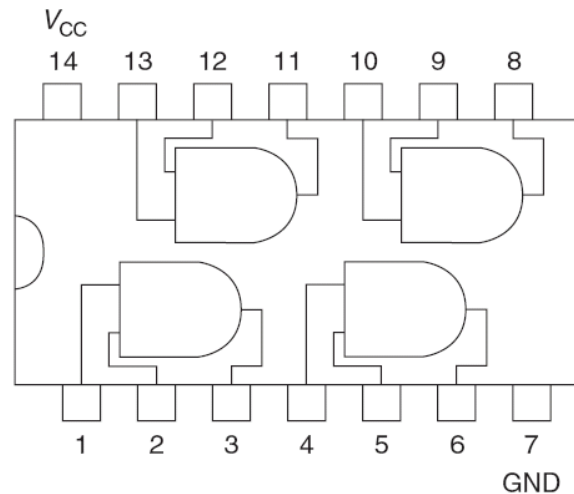


74LS08




Chip Logic Circuit (Cont.)

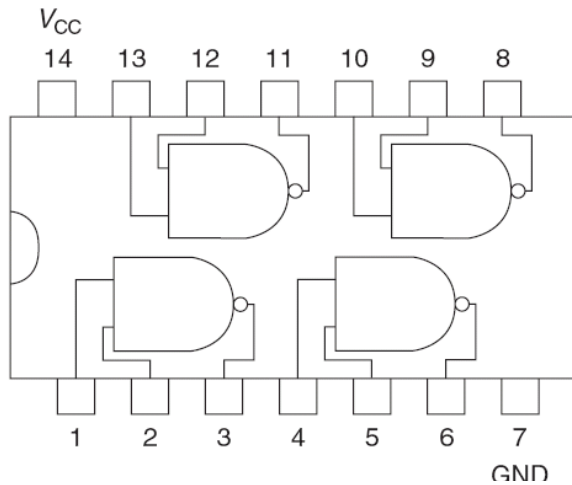

74LS00

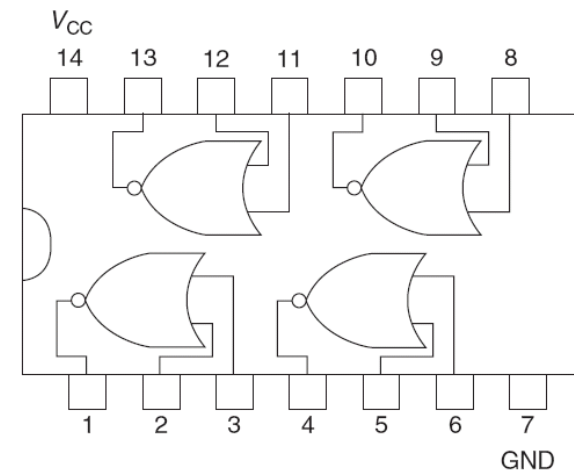

74LS02

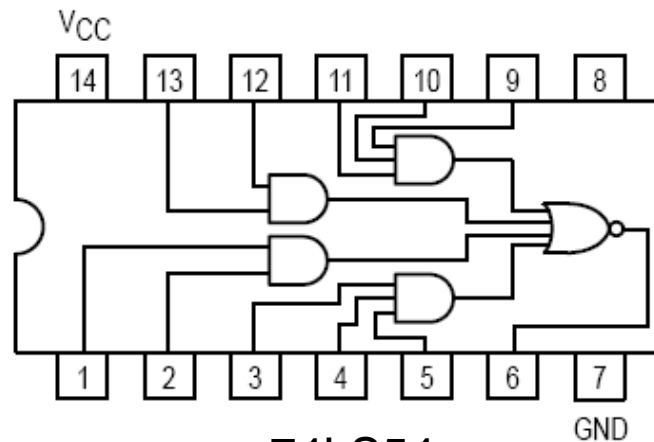

74LS54



Report 4 – Part 2

- 使用ALL-NAND 或 ALL-NOR 電路解決 Part 2 的問題並完成下圖中電路 (並標出所使用的IC編號，及導出邏輯線路的過程)。

- 說明所採用的電路及採用的原因。

