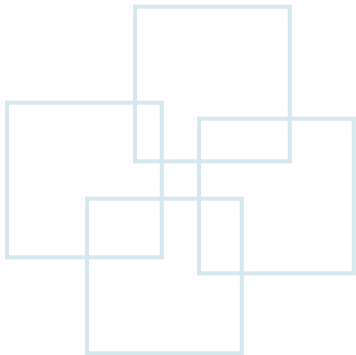





# Class 9

## Sequential Logic: Latch





# SR NAND Latch

   


| nS | nR | Q <sub>t+1</sub> | nQ <sub>t+1</sub> | Function  |
|----|----|------------------|-------------------|-----------|
| 0  | 0  | 1                | 1                 | Forbidden |
| 0  | 1  | 1                | 0                 | Set       |
| 1  | 0  | 0                | 1                 | Reset     |
| 1  | 1  | Q <sub>t</sub>   | nQ <sub>t</sub>   | No Change |

SR NAND Latch Function Table




# Reset-to-Set Transition


| nS | nR | $Q_{t+1}$ | $nQ_{t+1}$ | Function  |
|----|----|-----------|------------|-----------|
| 0  | 0  | 1         | 1          | Forbidden |
| 0  | 1  | 1         | 0          | Set       |
| 1  | 0  | 0         | 1          | Reset     |
| 1  | 1  | $Q_t$     | $nQ_t$     | No Change |

 

 
a) Stable in the RESET condition. Set and Reset inputs inactive.




b) Set input activates.

 

 
c) Change propagates through upper gate. (Either input LOW makes output HIGH.)



 
d) HIGH transfers across feedback line to lower gate, removing active input condition.



 e) Change propagates through lower gate. (Both inputs HIGH, therefore output LOW.)



 f) Feedback transfers LOW to upper gate, completing change to new state.




g) S input goes back to inactive state. SET state held by LOW at inner input of upper gate.




# Set-to-Reset Transition


| nS | nR | $Q_{t+1}$ | $nQ_{t+1}$ | Function  |
|----|----|-----------|------------|-----------|
| 0  | 0  | 1         | 1          | Forbidden |
| 0  | 1  | 1         | 0          | Set       |
| 1  | 0  | 0         | 1          | Reset     |
| 1  | 1  | $Q_t$     | $nQ_t$     | No Change |

 

 
a) Stable in the SET condition. Set and Reset inputs inactive.




b) Reset input activates.

 

 
c) Change propagates through lower gate. (Either input LOW makes output HIGH.)



 
d) HIGH transfers across feedback line to upper gate, removing active input condition.



 e) Change propagates through upper gate. (Both inputs HIGH, therefore output LOW.)



 f) Feedback line transfers LOW to lower gate, completing transition to RESET state.




g) R goes back to inactive level. Latch is stable in new state, held by the 0 on inner input of lower gate.




# Transition from Forbidden State


| nS | nR | $Q_{t+1}$ | $nQ_{t+1}$ | Function  |
|----|----|-----------|------------|-----------|
| 0  | 0  | 1         | 1          | Forbidden |
| 0  | 1  | 1         | 0          | Set       |
| 1  | 0  | 0         | 1          | Reset     |
| 1  | 1  | $Q_t$     | $nQ_t$     | No Change |

 

 
a) Both Set and Reset inputs active. Either input LOW makes output HIGH. Therefore, both outputs HIGH.



 
b) Set and Reset inputs deactivate simultaneously.



 
c) Change propagate through gates simultaneously.



 d) New output levels cross circuit via feedback lines.



 d) New output levels cross circuit via feedback lines.




f) Output logic levels cross circuit via feedback lines. Cycle repeats and circuit oscillates.




# Switch Bouncing

| nS | nR | $Q_{t+1}$ | $nQ_{t+1}$ | Function  |
|----|----|-----------|------------|-----------|
| 0  | 0  | 1         | 1          | Forbidden |
| 0  | 1  | 1         | 0          | Set       |
| 1  | 0  | 0         | 1          | Reset     |
| 1  | 1  | $Q_t$     | $nQ_t$     | No Change |

 

a. Pushbutton

 

b. Toggle



c. Ideal waveform




d. Effect of contact bounce




# Switch Debouncing

| nS | nR | $Q_{t+1}$ | $nQ_{t+1}$ | Function  |
|----|----|-----------|------------|-----------|
| 0  | 0  | 1         | 1          | Forbidden |
| 0  | 1  | 1         | 0          | Set       |
| 1  | 0  | 0         | 1          | Reset     |
| 1  | 1  | $Q_t$     | $nQ_t$     | No Change |

 

a. Switch debouncer

 



b. Timing diagram



# Gated SR NAND Latch


| nS | nR | $Q_{t+1}$ | $nQ_{t+1}$ | Function  |
|----|----|-----------|------------|-----------|
| 0  | 0  | 1         | 1          | Forbidden |
| 0  | 1  | 1         | 0          | Set       |
| 1  | 0  | 0         | 1          | Reset     |
| 1  | 1  | $Q_t$     | $nQ_t$     | No Change |

SR NAND Latch Truth Table

  

| EN | S | R | $Q_{t+1}$ | $nQ_{t+1}$ | Function  |
|----|---|---|-----------|------------|-----------|
| 1  | 0 | 0 | $Q_t$     | $nQ_t$     | No Change |
| 1  | 0 | 1 | 0         | 1          | Reset     |
| 1  | 1 | 0 | 1         | 0          | Set       |
| 1  | 1 | 1 | 1         | 1          | Forbidden |
| 0  | X | X | $Q_t$     | $nQ_t$     | Inhibited |


Gated NAND Latch Function Table

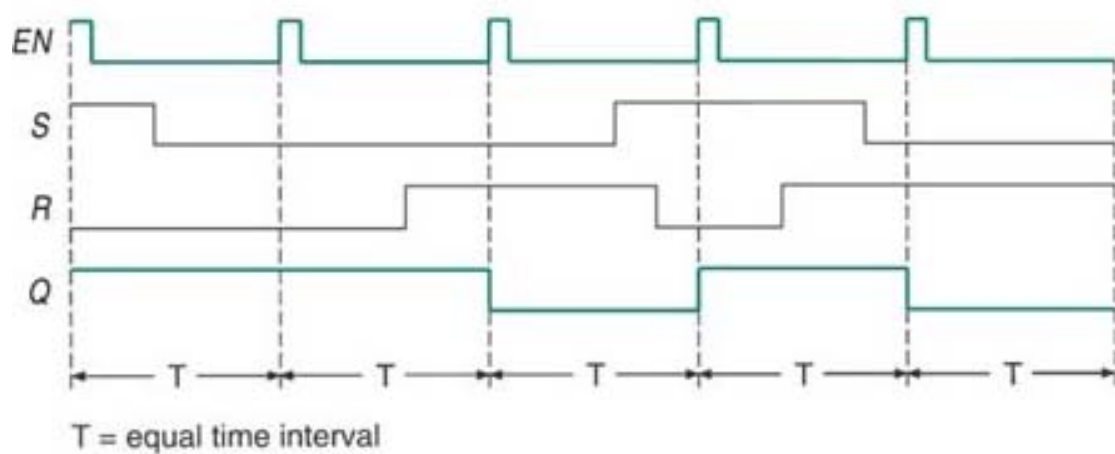






# Gated D Latch (Transparent Latch)

 

| EN | D | $Q_{t+1}$ | $nQ_{t+1}$ | Function  | Comment     |
|----|---|-----------|------------|-----------|-------------|
| 1  | 1 | 1         | 0          | Set       |             |
| 1  | 0 | 0         | 1          | Reset     | Transparent |
| 0  | X | $Q_t$     | $nQ_t$     | No Change | Store       |

Gated D Latch Function Table



 




# Gated D Latch (Cont.)

| nS | nR | $Q_{t+1}$ | $nQ_{t+1}$ | Function  |
|----|----|-----------|------------|-----------|
| 0  | 0  | 1         | 1          | Forbidden |
| 0  | 1  | 1         | 0          | Set       |
| 1  | 0  | 0         | 1          | Reset     |
| 1  | 1  | $Q_t$     | $nQ_t$     | No Change |

SR NAND Latch Truth Table

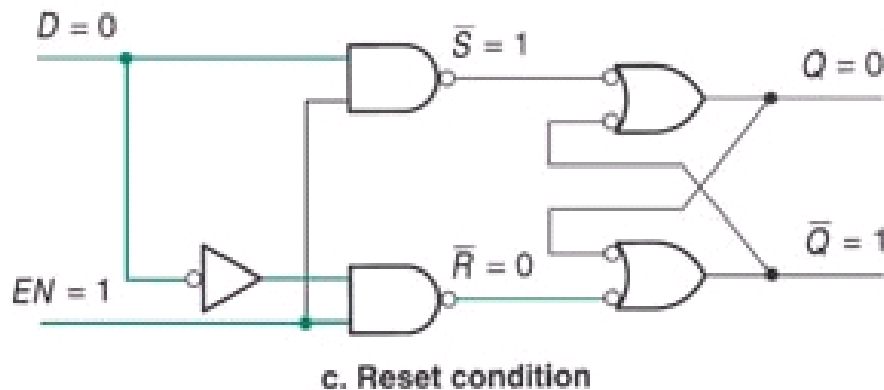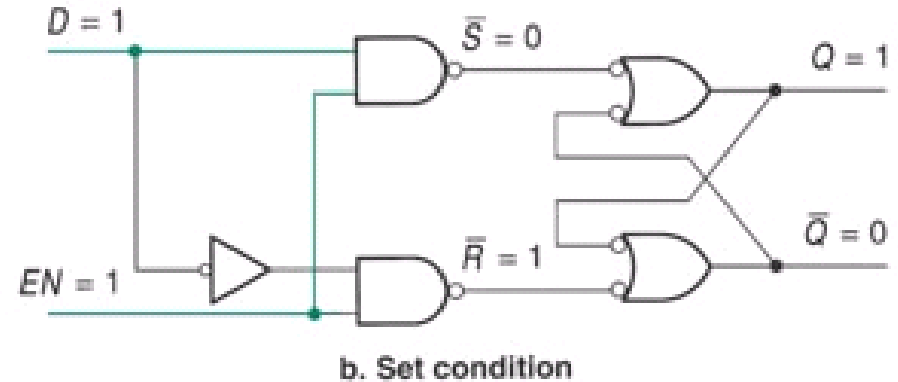 

| EN | D | $Q_{t+1}$ | $nQ_{t+1}$ | Function  | Comment     |
|----|---|-----------|------------|-----------|-------------|
| 1  | 1 | 1         | 0          | Set       |             |
| 1  | 0 | 0         | 1          | Reset     | Transparent |
| 0  | X | $Q_t$     | $nQ_t$     | No Change | Store       |

Gated D Latch Truth Table



# SR NAND Latch with VHDL


```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY nand_latch IS
  PORT
  (
    nS : IN STD_LOGIC;
    nR : IN STD_LOGIC;
    Q : OUT STD_LOGIC;
    nQ : OUT STD_LOGIC
  );
END nand_latch;

ARCHITECTURE bdf_type OF nand_latch IS
  SIGNAL wire0 : STD_LOGIC;
  SIGNAL wire1 : STD_LOGIC;
BEGIN

  Q <= wire1;
  nQ <= wire0;
  wire1 <= NOT(nS AND wire0);
  wire0 <= NOT(wire1 AND nR);

END bdf_type;
```

 



# Edge-Trigger Event

```

ENTITY counter IS
  PORT
  (
    Q: IN STD_LOGIC; -- reset counter
  );
END counter;

```

```


ARCHITECTURE a OF counter IS
  SIGNAL cnt: INTEGER RANGE 0 to 10;
BEGIN
  PROCESS(all)
  BEGIN
    IF (cnt > 9) THEN --reset digit
      cnt <= 0;
    ELSIF (Q'EVENT and Q='1') THEN -- Handle counter
      cnt <= cnt + 1;
    END IF;
  END PROCESS;
END a;

```

Sense everything port and signal

Integer can be used in addition, division, and comparison.

Q'EVENT and Q='0')

 

Q'EVENT and Q='1')

Event triggered at the rising edge of the Q signal



# Gated SR NAND Latch for Debouncing

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
ENTITY counter IS
    PORT
    (
        S, R, Enable : IN STD_LOGIC ; -- Latch's in input
        OnLed: OUT STD_LOGIC
    );
END counter;

ARCHITECTURE a OF counter IS
    SIGNAL Q,nQ : STD_LOGIC; -- debounced control signal
BEGIN

    -- Gated SR NAND latch to debounce pushbutton gitter
    Q <= ((not S) NAND Enable) NAND nQ;
    nQ <= ((not R) NAND Enable) NAND Q;
    OnLed <= Q ;

END a;
```



# Two-Digit Counter

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
ENTITY counter IS
    PORT(S : IN STD_LOGIC; -- Latch's in input);
END counter;
ARCHITECTURE a OF counter IS
    -- count the number of the button pressed
    SIGNAL digit0, digit1: INTEGER RANGE 0 to 16;
BEGIN
    pro0: PROCESS(S)
    BEGIN
        IF (S'EVENT and S='1') THEN -- Handle counter
            -- two-digit counter
            { digit0 <= digit0 + 1; -- advance the digit0 by one
              IF(digit0 >= 9) THEN
                  digit1 <= digit1 + 1;
                  digit0 <= 0;
                  IF(digit1 >= 9) THEN -- reset the digit1 to 0 (overflow)
                      digit1 <= 0;
                  END IF;
              END IF;
            END IF;
        END PROCESS pro0;
    END a;

```

Executed at the same time





## Lab 9

- **Note: This lab does not allow to use any existing latch modules.**
- Part 1: Gated SR NAND latch
  - Design a gated SR NAND latch.
  - Create a vector waveform file (.vwf) to evaluate the output of the latch.
    - S: count value, binary, simulation period=4us, advanced by 1 every 100ns, **start from 50ns**
    - R: count value, binary, simulation period=4us, advanced by 1 every 200ns, start from 0ns
    - EN: count value, binary, simulation period 4us, advanced by 1 every 2us, start from 0ns
- Part 2: **Gated SR NAND latch application**: Design the on/off pushbuttons with a counter
  - I/O Functions:
    - PushButton2 (**S**) is to turn on the motor (i.e., LED0: **Q**).
    - PushButton1 (**R**) is to turn off motor (i.e., LED0: **Q**).
    - PushButton0 is to reset the 2-digit BCD (or decimal) counter to 00.
    - Hex1 and Hex0 shows the value of the 2-digit BCD counter.
    - SW0 is to enable/disable the pushbuttons.
      - When SW0 is Logic-High, enable the pushbuttons. Otherwise, the pushbuttons are disabled.
  - The 2-digit BCD counter is advanced by one whenever the motor is turned ON from OFF (**rising-edge trigger**).



# Pushbutton and Slide Switches

Pin number

  

3 Pushbutton switches:  
 Not pressed → Logic High  
 Pressed → Logic Low

| Signal Name | FPGA Pin No. |
|-------------|--------------|
| BUTTON [0]  | PIN_ H2      |
| BUTTON [1]  | PIN_ G3      |
| BUTTON [2]  | PIN_ F1      |


10 Slide switches (Sliders):  
 Up → Logic High  
 Down → Logic

|       |         |       |         |
|-------|---------|-------|---------|
| SW[0] | PIN_ J6 | SW[5] | PIN_ J7 |
| SW[1] | PIN_ H5 | SW[6] | PIN_ H7 |
| SW[2] | PIN_ H6 | SW[7] | PIN_ E3 |
| SW[3] | PIN_ G4 | SW[8] | PIN_ E4 |
| SW[4] | PIN_ G5 | SW[9] | PIN_ D2 |





# LEDs

 

Pin number

10 LEDs


Output high → LED on  
Output low → LED off

| Signal Name | FPGA Pin No. |
|-------------|--------------|
| LEDG[0]     | PIN_J1       |
| LEDG[1]     | PIN_J2       |
| LEDG[2]     | PIN_J3       |
| LEDG[3]     | PIN_H1       |
| LEDG[4]     | PIN_F2       |
| LEDG[5]     | PIN_E1       |
| LEDG[6]     | PIN_C1       |
| LEDG[7]     | PIN_C2       |
| LEDG[8]     | PIN_B2       |
| LEDG[9]     | PIN_B1       |



# 7-Segment Displays

Pin number  
(active-low)

 

| Signal Name | FPGA Pin No. |
|-------------|--------------|
| HEX0_D[0]   | PIN_E11      |
| HEX0_D[1]   | PIN_F11      |
| HEX0_D[2]   | PIN_H12      |
| HEX0_D[3]   | PIN_H13      |
| HEX0_D[4]   | PIN_G12      |
| HEX0_D[5]   | PIN_F12      |
| HEX0_D[6]   | PIN_F13      |
| HEX0_DP     | PIN_D13      |

|           |         |
|-----------|---------|
| HEX1_D[0] | PIN_A13 |
| HEX1_D[1] | PIN_B13 |
| HEX1_D[2] | PIN_C13 |
| HEX1_D[3] | PIN_A14 |
| HEX1_D[4] | PIN_B14 |
| HEX1_D[5] | PIN_E14 |
| HEX1_D[6] | PIN_A15 |
| HEX1_DP   | PIN_B15 |

|           |         |
|-----------|---------|
| HEX2_D[0] | PIN_D15 |
| HEX2_D[1] | PIN_A16 |
| HEX2_D[2] | PIN_B16 |
| HEX2_D[3] | PIN_E15 |
| HEX2_D[4] | PIN_A17 |
| HEX2_D[5] | PIN_B17 |
| HEX2_D[6] | PIN_F14 |
| HEX2_DP   | PIN_A18 |

|           |         |
|-----------|---------|
| HEX3_D[0] | PIN_B18 |
| HEX3_D[1] | PIN_F15 |
| HEX3_D[2] | PIN_A19 |
| HEX3_D[3] | PIN_B19 |
| HEX3_D[4] | PIN_C19 |
| HEX3_D[5] | PIN_D19 |
| HEX3_D[6] | PIN_G15 |
| HEX3_DP   | PIN_G16 |