 




Class 11

Shift Registers







Serial Shift Register

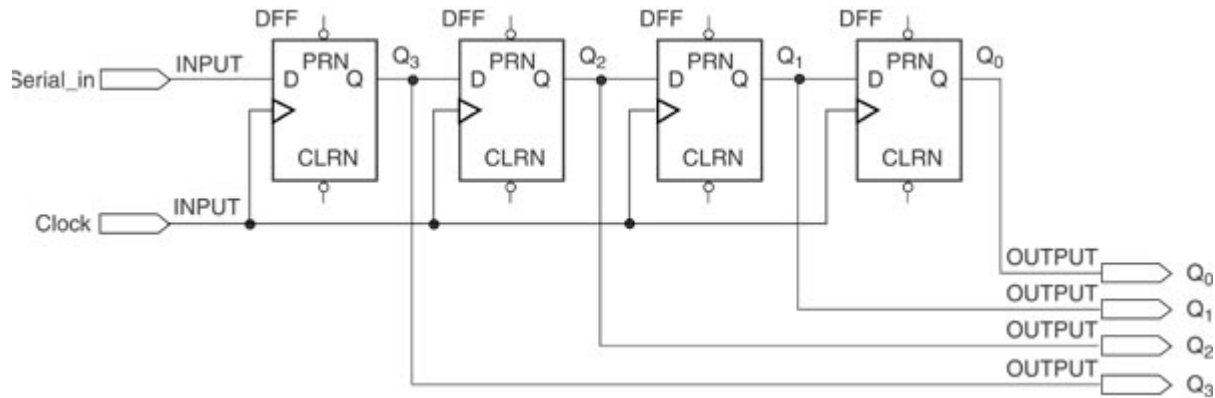 



Serial Shift Register (Cont.)

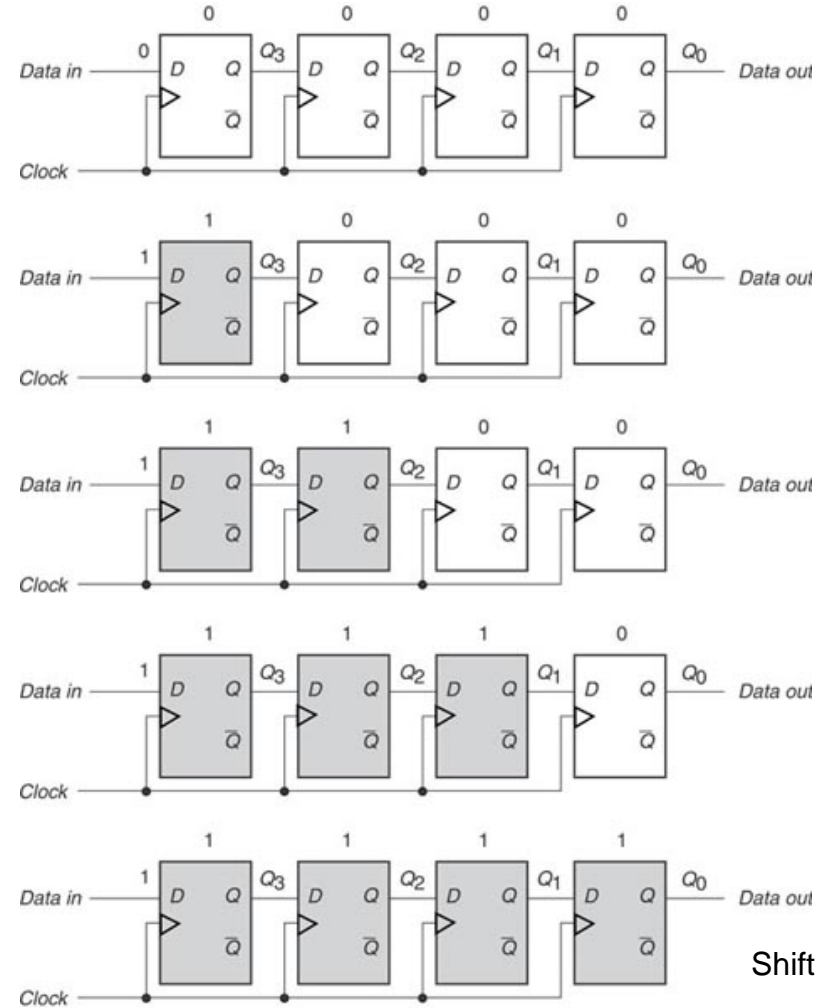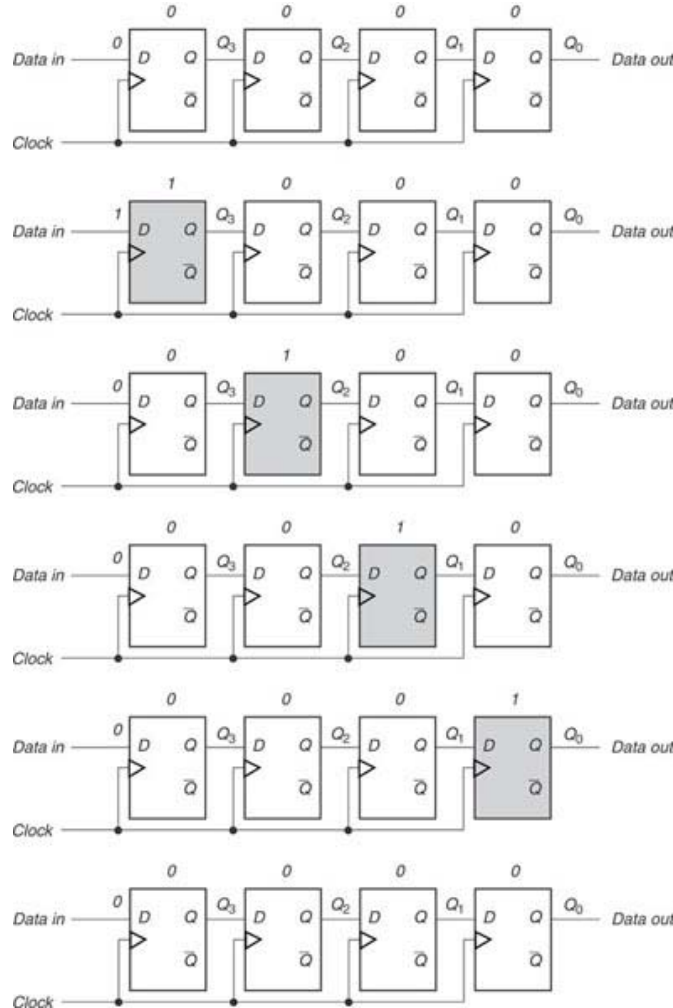

Shift a "1"

Shift with 1's



Universal Shift Register


S_1	S_0	Function	D_3	D_2	D_1	D_0
0	0	Hold	Q_3	Q_2	Q_1	Q_0
0	1	Shift Right	RSI	Q_3	Q_2	Q_1
1	0	Shift Left	Q_2	Q_1	Q_0	LSI
1	1	Load	P_3	P_2	P_1	P_0

RSI: Right-Shift Input
LSI: Left-Shift Input



Ring Counter

 - A serial shift register with feedback from the output of the last flip-flop to the input of the first.





Shift Register – Structural Design

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
LIBRARY altera;
USE altera.maxplus2.ALL;

ENTITY srg4strc IS
PORT(
  serial_in, clk : IN      STD_LOGIC;
  qo : BUFFER             STD_LOGIC_VECTOR(3
downto 0));
END srg4strc;

ARCHITECTURE right_shift of srg4strc IS
  COMPONENT dff
  PORT (d : IN STD_LOGIC;
        clk : IN STD_LOGIC;
        q : OUT STD_LOGIC);
  END COMPONENT;
BEGIN
  flip_flop_3: dff PORT MAP(serial_in, clk, qo(3));
  dffs: FOR i IN 2 downto 0 GENERATE
    flip_flops_2_to_0: dff PORT MAP (qo(i+1), clk, qo(i));
  END GENERATE;
END right_shift;

```


Include Altera packages for D Flip-Flop

BUFFER can be a feedback to the circuit

Declare the DFF component

Flip Flop 3

Flip Flop 2-0

 



Shift Register – Dataflow Design / Behavioral Design

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY srg4dfwl IS
  PORT(
    serial_in, clk : IN STD_LOGIC;
    q: BUFFER STD_LOGIC_VECTOR(3 downto 0));
END srg4dfwl;

ARCHITECTURE right_shift OF srg4dfwl IS
  SIGNAL d : STD_LOGIC_VECTOR(3 downto 0);
BEGIN
  PROCESS (clk)
  BEGIN
    -- Define a 4-bit D flip-flop
    IF (clk'EVENT and clk = '1') THEN
      q <= d;
    END IF;
  END PROCESS;
  d <= serial_in & q(3 downto 1);
END right_shift;
```

Dataflow design: describe a design entity in terms of the Boolean relationships between different parts of the circuit.

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY srg4behv IS
  PORT(
    serial_in, clk : IN STD_LOGIC;
    q: BUFFER STD_LOGIC_VECTOR(3 downto 0));
END srg4behv;

ARCHITECTURE right_shift OF srg4behv IS

BEGIN
  PROCESS (clk)
  BEGIN
    -- Define a 4-bit D flip-flop
    IF (clk'EVENT and clk = '1') THEN
      q <= serial_in & q(3 downto 1);
    END IF;
  END PROCESS;
END right_shift;
```

Behavioral design: describe a design entity in terms of the behavior of the circuit.



Shift Registers of Generic Width

Use the GENERIC clause to define a parameter

Default value is 4

Clear every bit of q() to '0'

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY srg4dfw IS
  GENERIC (width: POSITIVE := 4)
  PORT(
    serial_in, clk, clear : IN STD_LOGIC;
    q: BUFFER
      STD_LOGIC_VECTOR(width-1 downto 0));
END srg4dfw;
ARCHITECTURE right_shift OF srg4dfw IS
  SIGNAL d : STD_LOGIC_VECTOR(3 downto 0);
BEGIN
  PROCESS (clk)
  BEGIN
    IF (clear = '0') THEN
      q <= (others => '0'); -- clear every bit of q() to '0'
    ELSIF (clk'EVENT and clk = '1') THEN
      q <= d;
    END IF;
  END PROCESS;
  d <= serial_in & q(width-1 downto 1);
END right_shift;

```

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.std_logic_arith.ALL;
USE ieee.std_logic_unsigned.ALL;
ENTITY srg4dfw IS
  GENERIC (width: POSITIVE := 4)
  PORT(
    serial_in, clk, clear : IN STD_LOGIC;
    q: BUFFER
      STD_LOGIC_VECTOR(width-1 downto 0));
END srg4dfw;

ARCHITECTURE right_shift OF srg4dfw IS
BEGIN
  PROCESS (clk)
  BEGIN
    IF (clear = '0') THEN
      q <= CONV_STD_LOGIC_VECTOR(0, width);
    ELSIF (clk'EVENT and clk = '1') THEN
      q <= d;
    END IF;
  END PROCESS;
  d <= serial_in & q(width-1 downto 1);
END right_shift;

```




Possible Design Errors in PROCESS

- In VHDL, a PROCESS statement is *concurrent*, but statements inside the PROCESS are sequential.
 - Anything described by a PROCESS acts like a separate component in a design entity.
- Possible design errors:
 - Only one instance of the EVENT express (e.g., `clk'EVENT` and `clk='1'`) is allowed in a PROCESS statement.
 - No other port, signal, or variable is allowed to be included with the expression that evaluates the clock.
 - For the statements in a process, it is only possible to assign one value to a port, variable, or signal for each time the process executes.




Possible Design Errors in PROCESS (Cont.)

- Only one instance of the EVENT express (e.g., `clk'EVENT` and `clk='1'`) is allowed in a PROCESS statement.

```
PROCESS(clk)
BEGIN
  IF (clk'EVENT and clk='1') THEN
    IF (load='1') THEN
      q <= p;
    END IF;
  END IF;
  IF (clk'EVENT and clk='1') THEN
    IF (count_enable='1') THEN
      q <= q+1;
    END IF;
  END IF;
END PROCESS;
```

 Illegal syntax: more than
one clock per process



```
PROCESS(clk)
BEGIN
  IF (clk'EVENT and clk='1') THEN
    IF (load='1') THEN
      q <= p;
    ELSIF (count_enable='1') THEN
      q <= q+1;
    END IF;
  END IF;
END PROCESS;
```

Legal syntax




Possible Design Errors in PROCESS (Cont.)

- No other port, signal, or variable is allowed to be included with the expression that evaluates the clock.

```
PROCESS(clk)
BEGIN
  IF (clk'EVENT and clk='1' and load='1') THEN
    q <= p;
  ELSE
    q <= q+1;
  END IF;
END PROCESS;
```

 Illegal syntax: load evaluated in
same statement as clk



```
PROCESS(clk)
BEGIN
  IF (clk'EVENT and clk='1') THEN
    IF (load='1') THEN
      q <= p;
    ELSE
      q <= q+1;
    END IF;
  END IF;
END PROCESS;
```


Legal syntax



Possible Design Errors (Cont.)

- For the statements in a process, it is only possible to assign one value to a port, variable, or signal for each time the process executes.
 
```
PROCESS(clk)
BEGIN
  IF (clk'EVENT and clk='1') THEN
    IF (count_enable = '1') THEN
      q <= q+1;
    END IF;
    IF (load = '1') THEN
      q <= p;
    END IF;
    IF (clear = '0') THEN
      q <= (others =>'0');
    END IF;
  END IF;
END PROCESS;
```



```
PROCESS(clk)
BEGIN
  IF (clk'EVENT and clk='1') THEN
    IF (count_enable = '1') THEN
      q <= q+1;
    ELSIF (load = '1') THEN
      q <= p;
    ELSIF (clear = '0') THEN
      q <= (others =>'0');
    END IF;
  END IF;
END PROCESS;
```

Legal syntax

Ambiguous (but not illegal) syntax: q assigned more than once in a process. May have an unexpected result.





Lab 11

- Design a universal shift register with feedback from the output. The shift frequency is 5Hz.

PB₂	PB₁	Function	LED₉	LED₈	...	LED₁	LED₀
1	1	Hold	LED ₉	LED ₈	...	LED ₁	LED ₀
1	0	Shift Right	LED ₀	LED ₉	...	LED ₂	LED ₁
0	1	Shift Left	LED ₈	LED ₇	...	LED ₀	LED ₉
0	0	Load	SW ₉	SW ₈	...	SW ₁	SW ₀



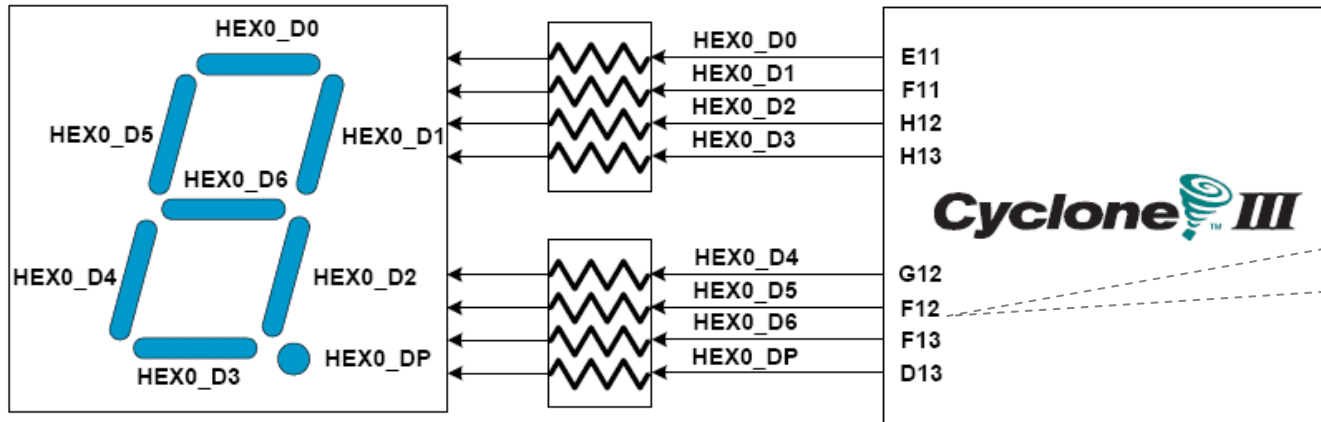 7-Segment Displays & DE0 – External Clock



Pin number
(active-low)

Signal Name	FPGA Pin No.
HEX0_D[0]	PIN_E11
HEX0_D[1]	PIN_F11
HEX0_D[2]	PIN_H12
HEX0_D[3]	PIN_H13
HEX0_D[4]	PIN_G12
HEX0_D[5]	PIN_F12
HEX0_D[6]	PIN_F13
HEX0_DP	PIN_D13

HEX1_D[0]	PIN_A13
HEX1_D[1]	PIN_B13
HEX1_D[2]	PIN_C13
HEX1_D[3]	PIN_A14
HEX1_D[4]	PIN_B14
HEX1_D[5]	PIN_E14
HEX1_D[6]	PIN_A15
HEX1_DP	PIN_B15



HEX2_D[0]	PIN_D15
HEX2_D[1]	PIN_A16
HEX2_D[2]	PIN_B16
HEX2_D[3]	PIN_E15
HEX2_D[4]	PIN_A17
HEX2_D[5]	PIN_B17
HEX2_D[6]	PIN_F14
HEX2_DP	PIN_A18

HEX3_D[0]	PIN_B18
HEX3_D[1]	PIN_F15
HEX3_D[2]	PIN_A19
HEX3_D[3]	PIN_B19
HEX3_D[4]	PIN_C19
HEX3_D[5]	PIN_D19
HEX3_D[6]	PIN_G15
HEX3_DP	PIN_G16



Pushbutton and Slide Switches

Pin number

  

3 Pushbutton switches:
 Not pressed → Logic High
 Pressed → Logic Low


Signal Name	FPGA Pin No.
BUTTON [0]	PIN_ H2
BUTTON [1]	PIN_ G3
BUTTON [2]	PIN_ F1

10 Slide switches (Sliders):
 Up → Logic High
 Down → Logic

SW[0]	PIN_ J6	SW[5]	PIN_ J7
SW[1]	PIN_ H5	SW[6]	PIN_ H7
SW[2]	PIN_ H6	SW[7]	PIN_ E3
SW[3]	PIN_ G4	SW[8]	PIN_ E4
SW[4]	PIN_ G5	SW[9]	PIN_ D2



LEDs

 

10 LEDs

Output high → LED on

Output low → LED off

Signal Name	FPGA Pin No.
LEDG[0]	PIN_J1
LEDG[1]	PIN_J2
LEDG[2]	PIN_J3
LEDG[3]	PIN_H1
LEDG[4]	PIN_F2
LEDG[5]	PIN_E1
LEDG[6]	PIN_C1
LEDG[7]	PIN_C2
LEDG[8]	PIN_B2
LEDG[9]	PIN_B1