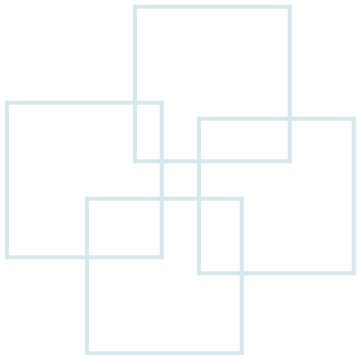


Class 13


Memory





Memory

 - A memory is a digital device or circuit that can store one or more bits of data.
- The simplest memory device is a **D-type latch** or a **D flip-flop**.




D-type latch

Output enable
(Read)

data_in:
8-bit data
input


Input gate enable
(Write)

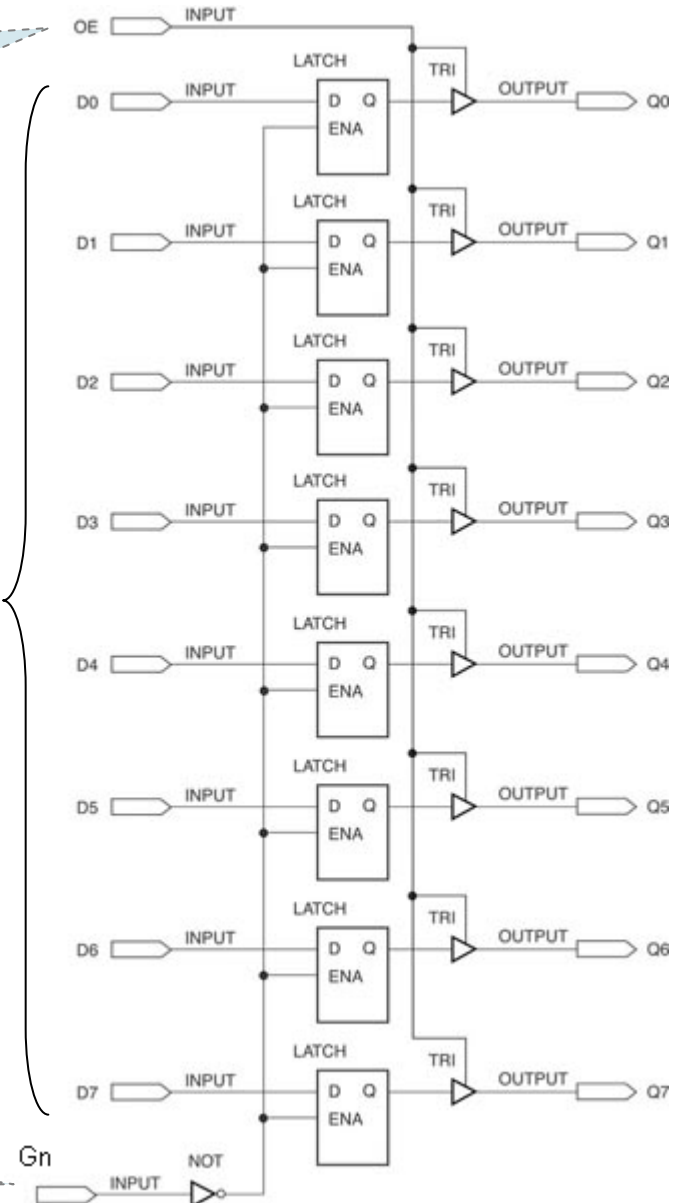




8-Bit Latch

Output enable
(Read)

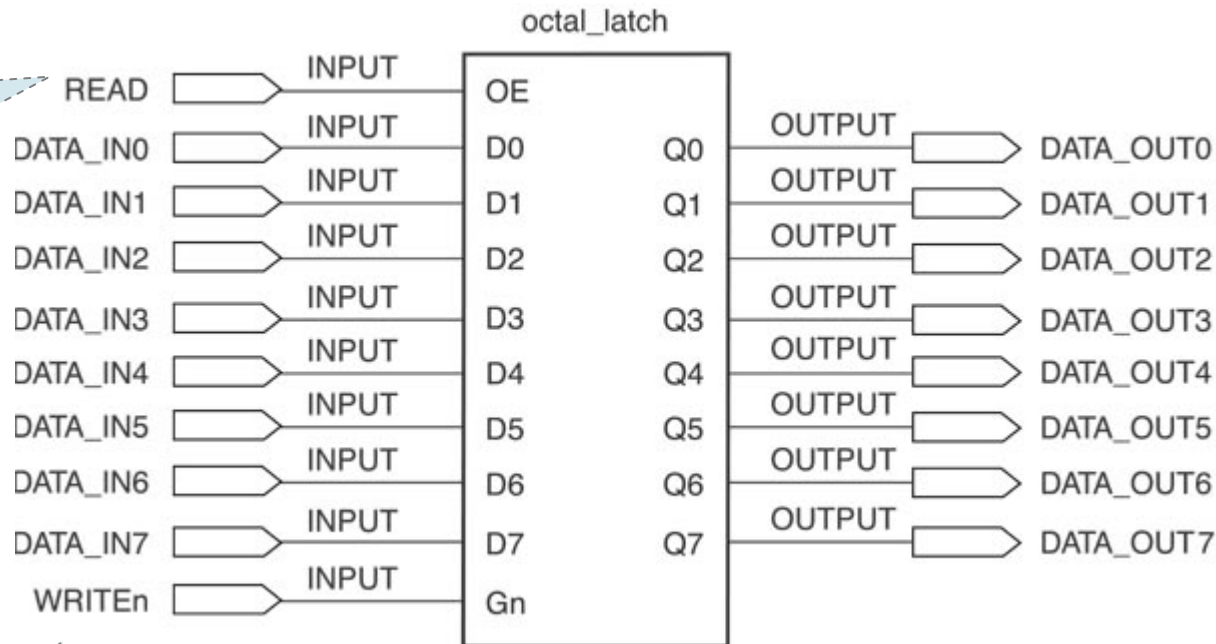


Input gate enable
(Write)

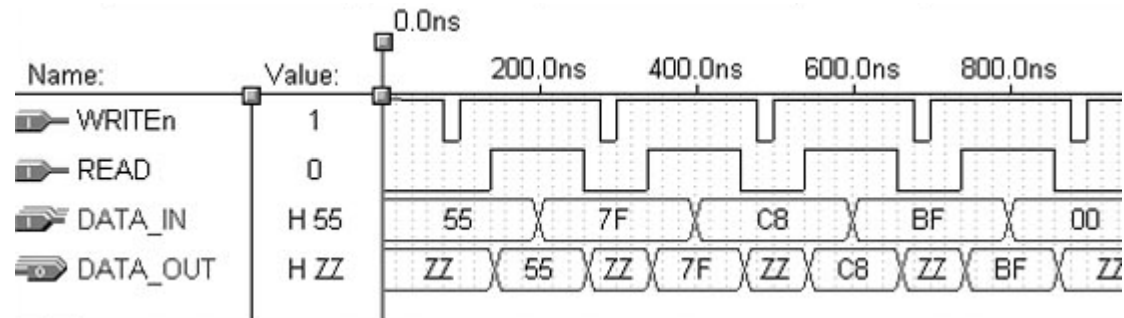



Address and Data Lines

 

a. Address and data lines

D_8		D_1	
1	0	1	1
0	0	0	1
1	1	0	1
0	0	0	0
0	1	1	1
1	0	0	0
0	1	0	1
0	1	0	1
1	0	1	0
0	1	0	1
1	1	0	1
0	0	0	1
1	1	0	0
1	1	0	1
1	1	0	1

b. Contents (data) and location (address)

Addresses				
Binary				
Hexadecimal				
0	0000	0000	0000	0000
0	0000	0000	0001	0001
0	0000	0000	0010	0002
0	0000	0000	0011	0003
0	0000	0000	0100	0004
0	0000	0000	0101	0005
0	0000	0000	0110	0006
⋮				⋮
1	1111	1111	1101	1FFD
1	1111	1111	1110	1FFE
1	1111	1111	1111	1FFF


8K x 8 Memory
 Address: $2^{13} = 8192$ WORD
 Data: 8 bits (= 1 WORD)

$addr(0) = "10110101"$, when $A_{12} \dots A_0 = 000000000000 = 0x000$
 $addr(1) = "00011011"$, when $A_{12} \dots A_0 = 000000000001 = 0x001$



Address, Data, and Control Signals

Address lines

 


a. 1K x 4 RAM

Low: Write
High: Read

Output enable


Chip enable

 

b. 1K x 8 ROM (EPROM)



Memory Control Signals

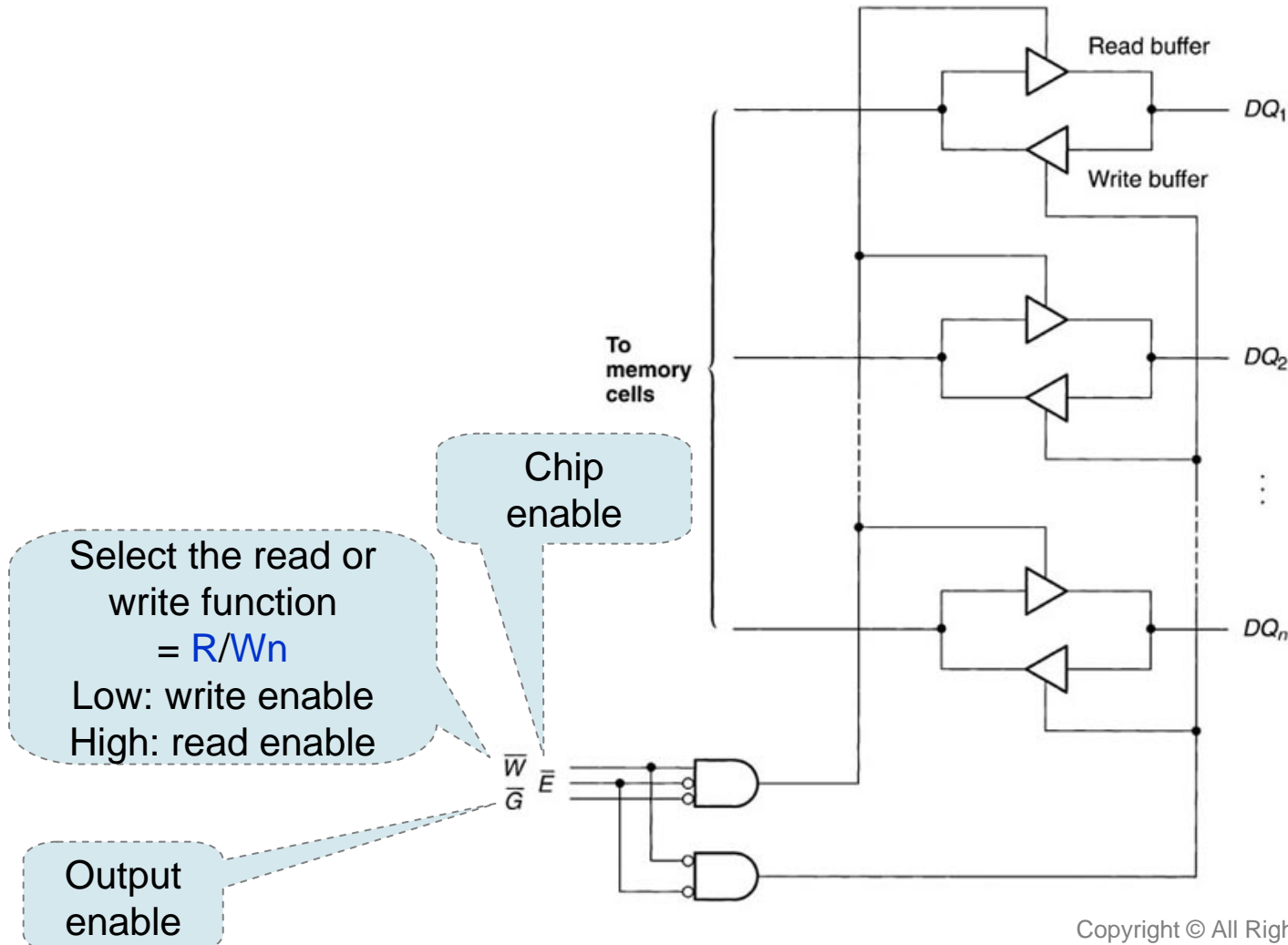



64x4bit Memory - Behavioral Design

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_unsigned.all;
USE ieee.std_logic_arith.all;

ENTITY Memory IS
  PORT(
    SlideSwitch: IN STD_LOGIC_VECTOR(9 downto 0);
    PushButton: IN STD_LOGIC_VECTOR(2 downto 0);
    Output: OUT STD_LOGIC_VECTOR(7 downto 0));
END Memory;

ARCHITECTURE memory OF Memory IS
  CONSTANT MAX_ADDR: INTEGER := 64;
  CONSTANT BUS_WIDTH: INTEGER := 4;
  SIGNAL addr: STD_LOGIC_VECTOR(5 downto 0);
  SIGNAL data_in: STD_LOGIC_VECTOR(BUS_WIDTH-1 downto 0);
  SIGNAL CEn, Wn, OEn: STD_LOGIC;
  TYPE MEMORY_ARRAY IS array(0 to MAX_ADDR-1) OF
    STD_LOGIC_VECTOR(BUS_WIDTH-1 downto 0);
  SIGNAL sram: MEMORY_ARRAY;
BEGIN
  -- port mapping
  addr <= SlideSwitch(9 downto 4);
  data_in <= SlideSwitch(3 downto 0);
  CEn <= PushButton(0);
  Wn <= PushButton(1);
  OEn <= PushButton(2);

```

Declare an 4x8bit SRAM

```

PROCESS(ALL)
  BEGIN
    -- Memory
    IF(CEn = '0') THEN -- chip enabled
      IF(Wn = '0') THEN -- Write enable
        sram(conv_integer(addr)) <= data_in;
        Output <= (others => '1');
      ELSIF(OEn='0') THEN -- Read enable and output enable
        Output <= sram(conv_integer(addr));
      ELSE
        Output <= (others => '1');
      END IF;
    ELSE
      Output <= (others => '1');
    END IF;
  END PROCESS;
END memory;

```

During the write operation, output is disabled

Read data from the selected address to the output port

Write input data to the selected address

Convert std_logic_vector to integer (need to include USE ieee.std_logic_unsigned.all; USE ieee.std_logic_arith.all;)

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_unsigned.all;
USE ieee.std_logic_arith.all;

...
SIGNAL a: STD_LOGIC_VECTOR(7 downto 0);
SIGNAL b: INTEGER RANGE 0 to 255;
a <= conv_std_logic_vector(b, 8);
b <= conv_integer(a);

```

Convert b into a 8-bit std_logic_vector

Convert a into an integer.



Counter Array with Fast Increments

```

ARCHITECTURE memory OF Memory IS
  CONSTANT TicksPerMilliSecond: INTEGER := 50000;
  CONSTANT DebounceTime: INTEGER := TicksPerMilliSecond * 5;
  CONSTANT FastCountDelay: INTEGER := TicksPerMilliSecond * 1000;
  CONSTANT FastCountInterval: INTEGER := TicksPerMilliSecond * 100;
  CONSTANT MAX_COUNTER: INTEGER := 4;
  TYPE COUNTER_ARRAY IS array(0 to MAX_COUNTER-1) OF INTEGER;
  SIGNAL PressedTime: NATURAL := 0;
  SIGNAL cnt: COUNTER_ARRAY;
  SIGNAL cnt_addr: STD_LOGIC_VECTOR(3 downto 0);
BEGIN
  PROCESS(ALL)
  BEGIN
    -- counters
    IF(clk'EVENT and clk = '1') THEN
      IF(CNTn='0') THEN
        IF(PressedTime < DebounceTime) THEN
          PressedTime <= PressedTime + 1; -- Wait for debounce time
        ELSIF(PressedTime = DebounceTime) THEN
          PressedTime <= PressedTime + 1; -- Debounce time is reached
          cnt(conv_integer(cnt_addr)) <= cnt(conv_integer(cnt_addr)) + 1;
        ELSE -- fast and accumulated counting
          PressedTime <= PressedTime + 1; -- Keep accumulating the pressed time
          IF(PressedTime = FastCountDelay+FastCountInterval) THEN -- Reach the fast count point
            cnt(conv_integer(cnt_addr)) <= cnt(conv_integer(cnt_addr)) + 1;
            PressedTime <= FastCountDelay; -- Reset the pressed time to wait for the next delay
          END IF;
        END IF;
      ELSE
        PressedTime <= 0;
      END IF;
      -- reset counter
      IF(cnt(conv_integer(cnt_addr)) >9) THEN
        cnt(conv_integer(cnt_addr)) <= 0;
      END IF;
    END IF;
  END PROCESS;
END memory;

```

Define a data structure with 16 integers


Declare an array with 16 counters

Wait until the debouncing time is reached

Wait until the fast increment time is reached





Lab 13

 

- Design a 4x8bit memory.
 - $addr[1..0]$ is mapped to $SW[9..8]$ (SlideSwitch);
 - $data_in[7..0]$ is mapped to $SW[7..0]$;
 - $DQ[7..0]$ is converted into two-hexadecimal digits shown in $Hex[1..0]$ (7-segments).
 - En (chip enable) is mapped to $PushButton[0]$
 - R/Wn (read/write selection) is mapped to $PushButton[1]$;
 - OEn (or Gn: output enable) is mapped to $PushButton[2]$;
- Design an array of 16 counters with fast increment support
 - Each counter is a two-digit counter that counts from 0 to 99.
 - Each counter is selected by the decoded value of $SW[3..0]$.
 - When a counter is selected, its content is shown in $Hex[3..2]$.
 - When $PushButton[1]$ is pushed, the selected counter is advanced by one.
 - If $PushButton[1]$ is pushed for more than one second, the selected counter is advanced by one every 100ms.



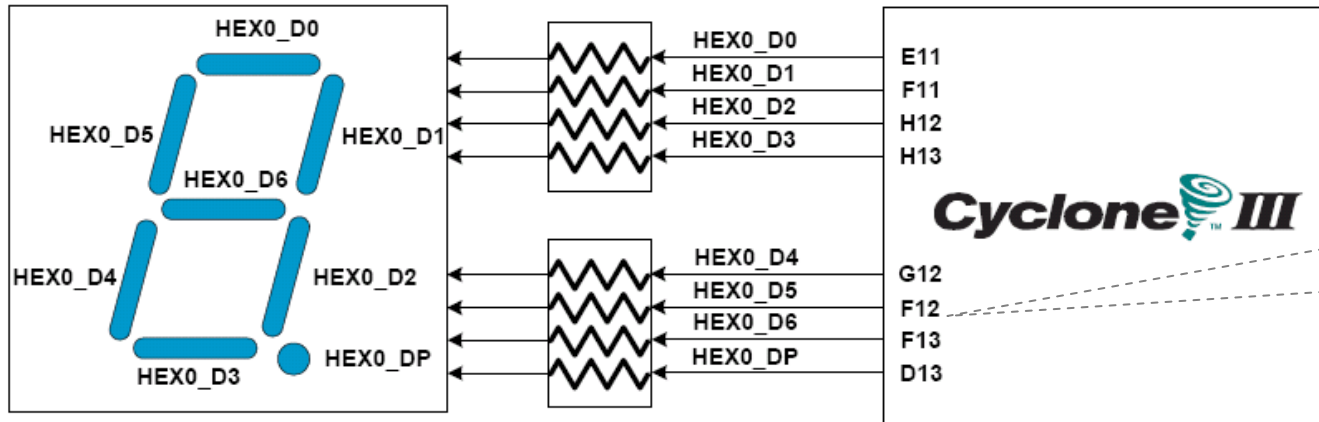 7-Segment Displays & DE0 – External Clock



Pin number
(active-low)

Signal Name	FPGA Pin No.
HEX0_D[0]	PIN_E11
HEX0_D[1]	PIN_F11
HEX0_D[2]	PIN_H12
HEX0_D[3]	PIN_H13
HEX0_D[4]	PIN_G12
HEX0_D[5]	PIN_F12
HEX0_D[6]	PIN_F13
HEX0_DP	PIN_D13

HEX1_D[0]	PIN_A13
HEX1_D[1]	PIN_B13
HEX1_D[2]	PIN_C13
HEX1_D[3]	PIN_A14
HEX1_D[4]	PIN_B14
HEX1_D[5]	PIN_E14
HEX1_D[6]	PIN_A15
HEX1_DP	PIN_B15



HEX2_D[0]	PIN_D15
HEX2_D[1]	PIN_A16
HEX2_D[2]	PIN_B16
HEX2_D[3]	PIN_E15
HEX2_D[4]	PIN_A17
HEX2_D[5]	PIN_B17
HEX2_D[6]	PIN_F14
HEX2_DP	PIN_A18

HEX3_D[0]	PIN_B18
HEX3_D[1]	PIN_F15
HEX3_D[2]	PIN_A19
HEX3_D[3]	PIN_B19
HEX3_D[4]	PIN_C19
HEX3_D[5]	PIN_D19
HEX3_D[6]	PIN_G15
HEX3_DP	PIN_G16



Pushbutton and Slide Switches

Pin number

  

3 Pushbutton switches:
 Not pressed → Logic High
 Pressed → Logic Low


Signal Name	FPGA Pin No.
BUTTON [0]	PIN_ H2
BUTTON [1]	PIN_ G3
BUTTON [2]	PIN_ F1

10 Slide switches (Sliders):
 Up → Logic High
 Down → Logic


SW[0]	PIN_J6	SW[5]	PIN_J7
SW[1]	PIN_H5	SW[6]	PIN_H7
SW[2]	PIN_H6	SW[7]	PIN_E3
SW[3]	PIN_G4	SW[8]	PIN_E4
SW[4]	PIN_G5	SW[9]	PIN_D2



LEDs

 

Pin number

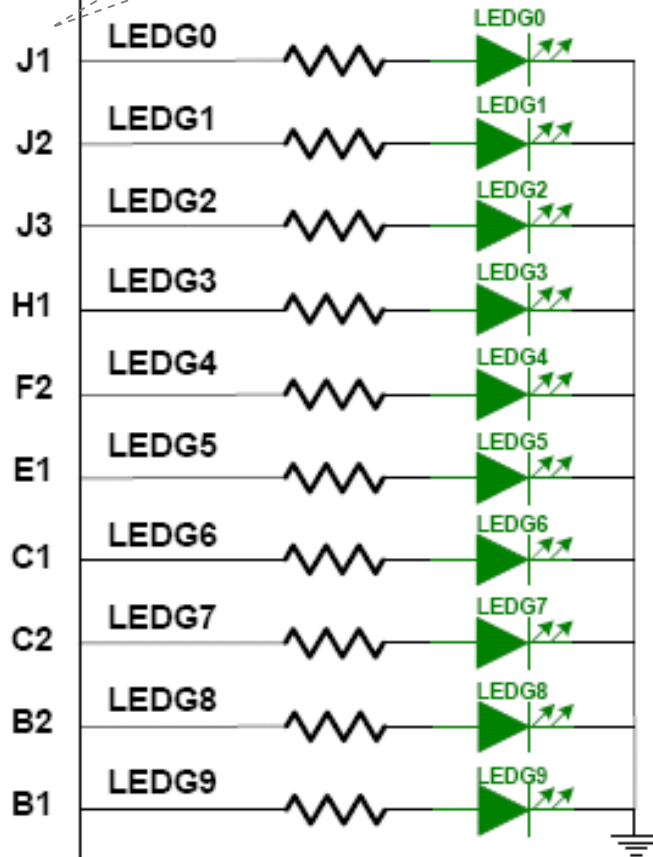

10 LEDs
 Output high → LED on
 Output low → LED off

Signal Name	FPGA Pin No.
LEDG[0]	PIN_J1
LEDG[1]	PIN_J2
LEDG[2]	PIN_J3
LEDG[3]	PIN_H1
LEDG[4]	PIN_F2
LEDG[5]	PIN_E1
LEDG[6]	PIN_C1
LEDG[7]	PIN_C2
LEDG[8]	PIN_B2
LEDG[9]	PIN_B1